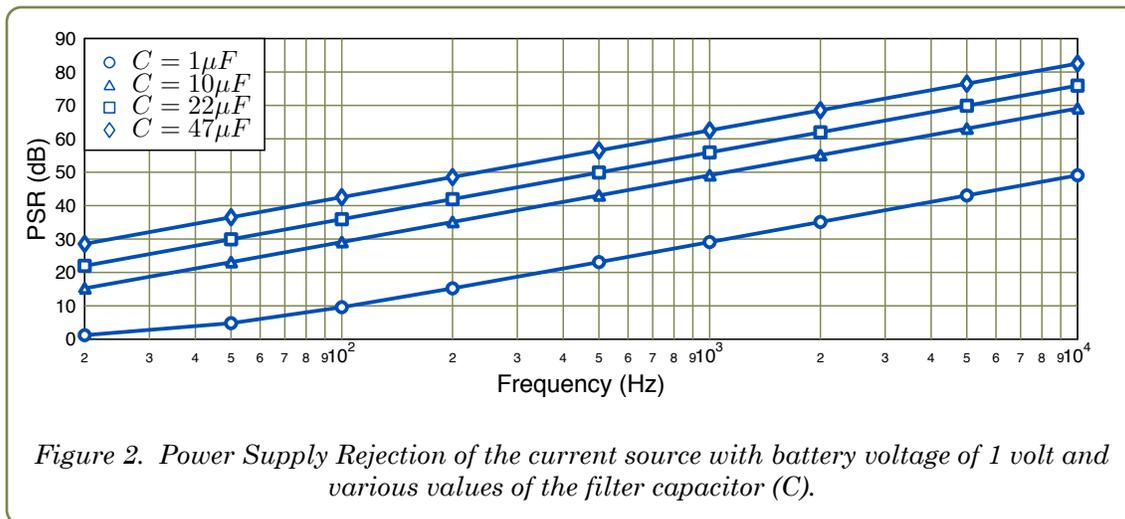


Many Knowles microphones require three terminal connections, one each for supply voltage and ground, and a third for the output signal from the microphone. A Knowles two-wire microphone has only two terminal connections, where the supply and signal are on the same pin. The microphone is powered by a current source, and the output signal is separated from the current source through a coupling capacitor (C_c).

For optimum performance, an active current source (*i.e.*, composed of matched bipolar or MOS transistors) should be used. However,

satisfactory performance for many applications can be obtained with passive components using the circuit in Figure 1.

The Knowles two-wire microphone requires 20 μA (nominal), and the recommended minimum compliance of the current source driving it is 0.9 V to insure maximum peak-to-peak output voltage. Power Supply Rejection (PSR) is a factor since the passive current source is connected directly to the hearing instrument battery. Figure 2 shows the PSR for various values of filter capacitor (C). The maximum capacitance values for a given form factor and



dielectric type are in Table 1. As an example, for a PSR of 40 dB at 200 Hz, choose a 22 μ F capacitor; this value is available in a 0805 for ceramic or a 0603 for tantalum.

The graphs in Figure 2 were generated from simulations. It is recommended that prototype circuits be evaluated prior to incorporation into a hearing instrument. Knowles Electronics can provide assistance if desired in the design and component selection for a particular application.

Capacitor Size	Ceramic	Tantalum
0402	1 μ F	not available
0603	10 μ F	22 μ F
0805	22 μ F	not available
1206	22 μ F	47 μ F

Table 1. Maximum capacitor values for different package sizes and dielectric types.

KNOWLES ELECTRONICS, LLC
 1151 MAPLEWOOD DRIVE
 ITASCA, ILLINOIS 61034
 USA
 +1 630 250 5100 VOICE
 +1 630 250 0575 FAX
 WWW.KNOWLESELECTRONICS.COM

KNOWLES EUROPE
 YORK ROAD, BURGESS HILL
 WEST SUSSEX, RH15 9TT
 ENGLAND
 +44 1444 235432 VOICE
 +44 1444 248724 FAX

KNOWLES ELECTRONICS, SUZHOU
 #179 SUHONG ROAD
 SUZHOU INDUSTRIAL PARK
 SUZHOU, JIANGSU 215021
 CHINA
 +86 512 6258 8258 VOICE
 +86 512 6258 9258 FAX

KNOWLES ELECTRONICS (M) SDN.
 BHD.
 PLOT 104
 LEBUHRAYA KAMPUNG JAWA
 GEORGETOWN, PENANG 11900
 MAYLASIA
 +60 4 6437 466 VOICE
 +60 4 6437 446 FAX

KNOWLES ELECTRONICS, JAPAN
 5/F YK BUILDING 2-16
 SANGENJAYA 2-CHOME
 SETAGAYA-KY, TOKYO 154-0024
 JAPAN
 +81 3 3439 1151 VOICE
 +81 3 3439 8822 FAX

MICROMAX PTY LTD
 5 ORANGEGROVE AVENUE
 UNANDERRA NSW 2526
 AUSTRALIA
 +61 2 4271 1300 VOICE
 +61 2 4271 8091 FAX
 WWW.MICROMAX.COM.AU

Note: All data and performance specifications in this document are for reference only.